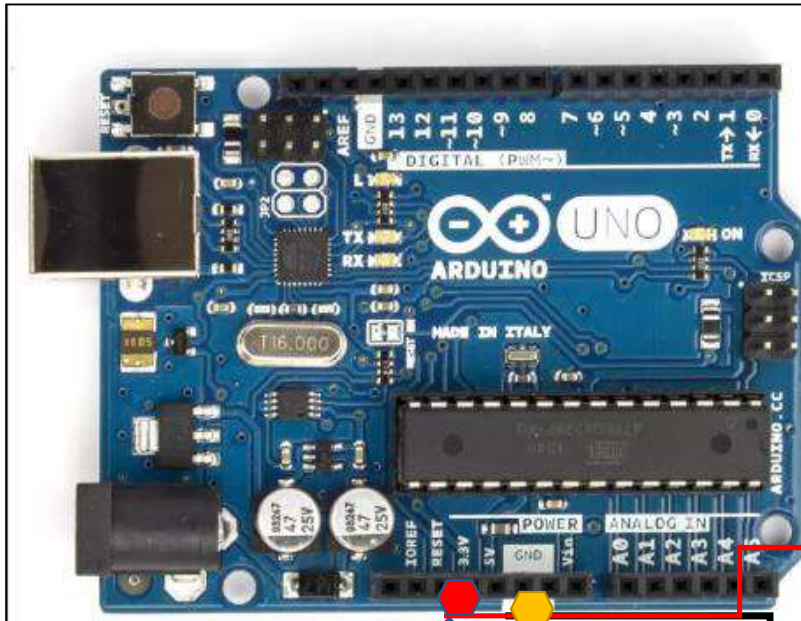


Build the 'Rockstar' circuit


Assemble our circuit – UNO + TEA5767



Arduino	TEA5767
A4	SDA
A5	SCL
3.3V	VCC
GND	GND



Assemble the circuit – UNO + SWITCH

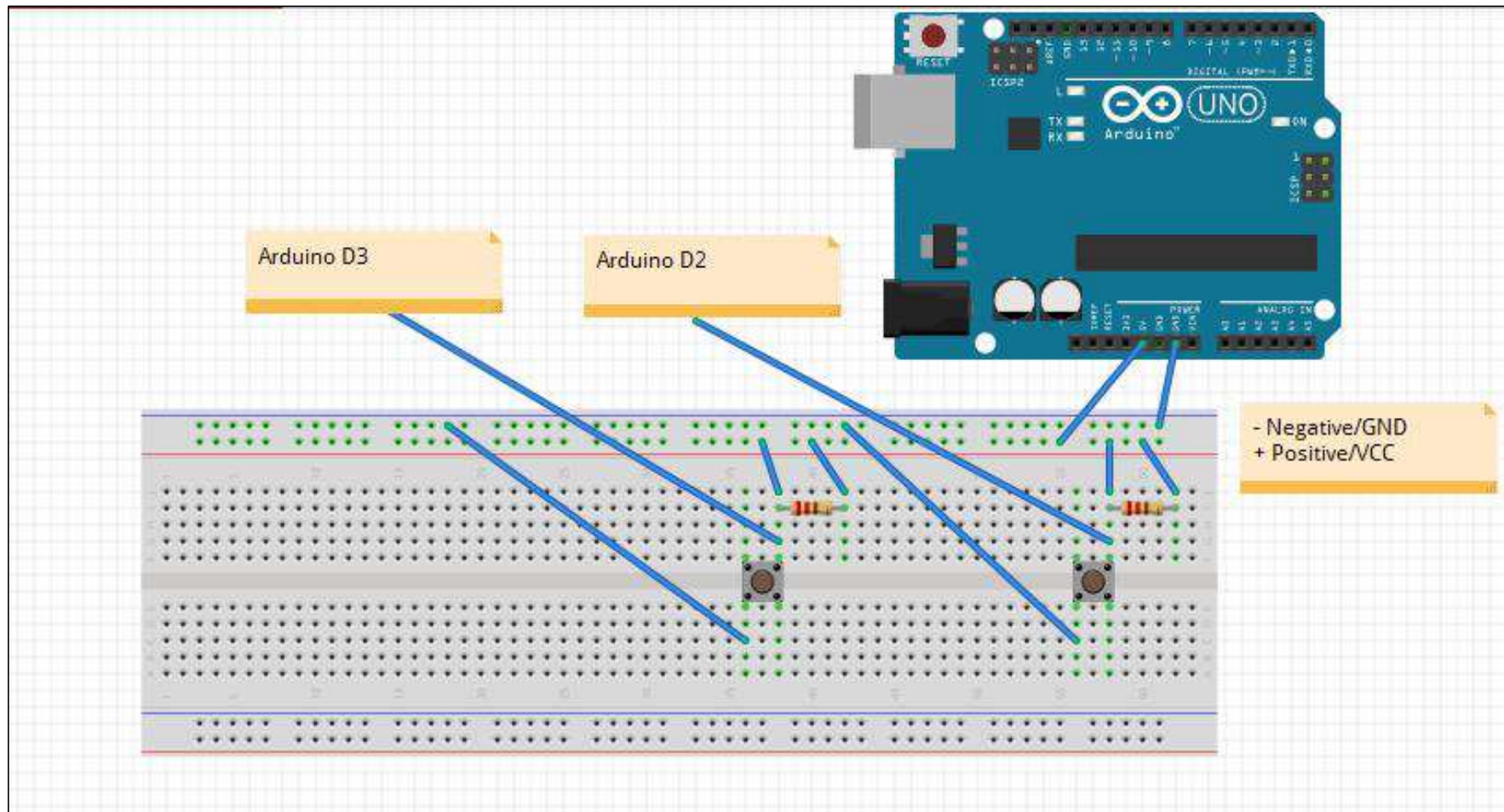

Test our project

1. Open Serial monitor and make sure Baud rate is 115200
2. Press Arduino reset button if nothing happens
3. Push up the channel switch to change channel
4. Test the mute button and press again to unmute